



The above circuit represents the series of patches made to a power supply over time. As the load changes, so did the power supply requirements. Before this turns into even more of a mess, your boss asked you to come up with a simpler design that will accomplish the same job. The simpler design must use fewer components and work exactly the same no matter what the load is. Design an equivalent circuit that does the job.