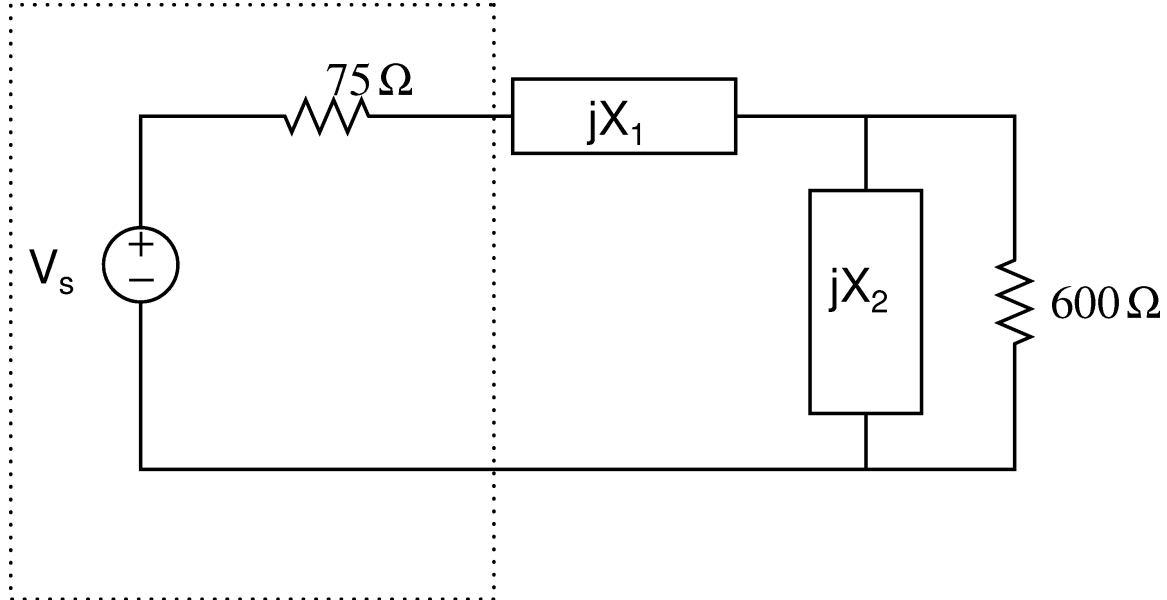


Modification of 8-65



The above represents an AC circuit design for balancing a load in AC. The only power supply available has an internal resistance of  $75\ \Omega$ . The load has a resistance of  $600\ \Omega$ . You want to deliver the maximum power possible to the load. By properly selecting  $X_1$  and  $X_2$ , one can deliver the maximum amount of power to the load. This is done by making the source's output impedance look like  $75 + 0j\ \Omega$ . Select  $X_1$  and  $X_2$  to accomplish this.

Once this is done, select the capacitors and inductors needed at  $\omega = 10^6$  rad/s.